

For the inductor L , assume the current through it is

$$i = I_m \cos(\omega t + \phi)$$

The voltage across the inductor is

$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

We can write the voltage as

$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

which transforms to the phasor

$$V = \omega L I_m e^{j(\phi+90^\circ)} = \omega L I_m e^{j\phi} e^{j90^\circ} = \omega L I_m \angle \phi + 90^\circ$$

As

$$e^{j90^\circ} = j$$

$$V = j\omega L I$$

In the preceding section, we obtained the voltage-current relations for the three passive elements as

$$V = RI, \quad V = j\omega LI, \quad V = \frac{I}{j\omega C}$$

\mathbf{Z} is a frequency-dependent quantity known as *impedance*, measured in ohms.

Table 5.2
Impedances and admittances
of passive elements.

Element	Impedance	Admittance
R	$\mathbf{Z} = R$	$\mathbf{Y} = \frac{1}{R}$
L	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = \frac{1}{j\omega L}$
C	$\mathbf{Z} = \frac{1}{j\omega C}$	$\mathbf{Y} = j\omega C$

As a complex quantity, the impedance may be expressed in rectangular form as

$$Z = R + jX$$

Or

$$Z = |Z| \angle \theta$$

where

$$|Z| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

Find $v(t)$ and $i(t)$ in the circuit shown in Figure 5.2.

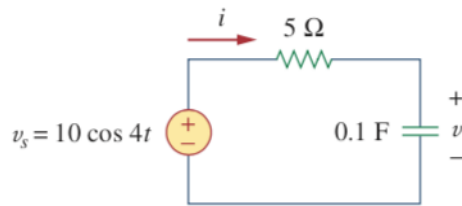


Figure 5.2

Solution:

From the voltage source,

$$10 \cos 4t, \omega = 4$$
$$V_s = 10 \angle 0^\circ \text{ V}$$

The impedance is

$$Z = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \Omega$$

Hence the current

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5 - j2.5} = \frac{10(5 + j2.5)}{5^2 + 2.5^2}$$
$$= 1.6 + j0.8 = 1.789 \angle 26.57^\circ \text{ A}$$

The voltage across the capacitor is

$$V = IZ_C = \frac{I}{j\omega C} = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1}$$
$$= \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ} = 4.47 \angle -63.43^\circ \text{ V}$$

Converting **I** and **V** to the time domain, we get

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$
$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Notice that $i(t)$ leads $v(t)$ by 90 as expected.